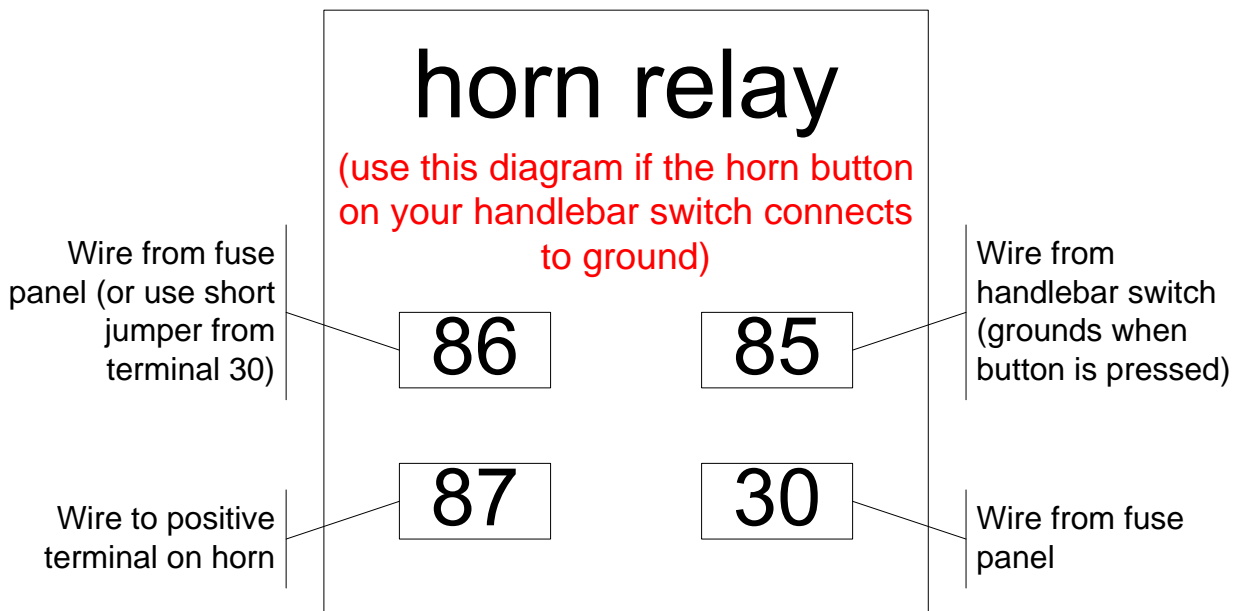


Adding a relay to operate horn(s)

This approach uses relays to provide positive current to the horn(s). Horn(s) must be grounded.

This diagram is applicable to most Moto Guzzi handlebar switches.



Use one or the other, but not both diagrams

This diagram is NOT applicable to most Moto Guzzi handlebar switches.

