

# Adding relays to operate high and low beam headlights

I like to use separate relays for the high and low beam circuits. That way, if one relay fails, I still have lights.

